

# Robotics, Teaching & Learning

Philippe Lucidarme

## Commutation sequence for BLDC motors using Hall effect position sensors

🕒 May 30, 2014   📁 Programming   👤 admin

Conmutación de un motor brushless DC multipolar (BLDC)



The following diagram shows a simplify overview of the BLDC motor controller. The motor inputs are the three phase and the motor provides as output the binary data from three hall effect position sensors. The phases are driven by three H-Bridge (usually made of transistors but simplified here as switches). Each switch is driven by the microcontroller outputs (Q1H, Q1L, Q2H, Q2L, Q3H and Q3L). In the following we will assume that the switches are closed (on) when the signal from the microcontroller is high (for exemple QL1\_bit=1 => QL1 is closed => Phase 1 is connected to the ground). In the same way, we will assume that the hall effect sensors are active high.




**All components are from authorized distributors!**  
Reliable PCBA service for small&medium volume.




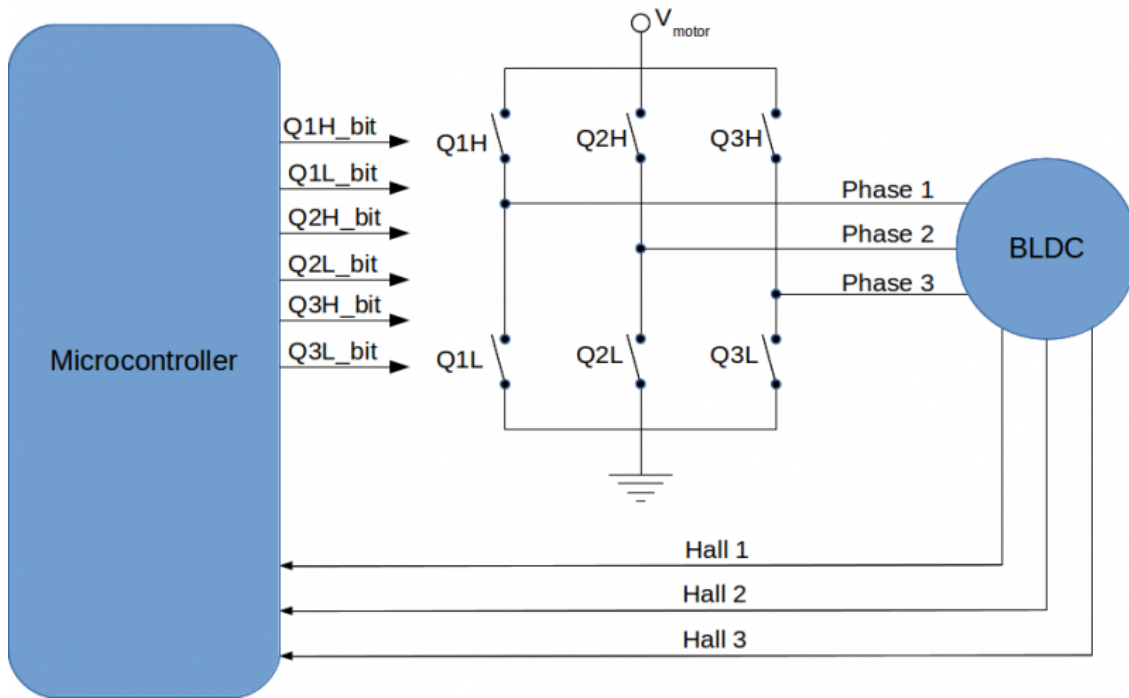**Order Now**

We use cookies to ensure that we give you the best experience on our website. If you continue to use this site we will assume that you are happy with it.



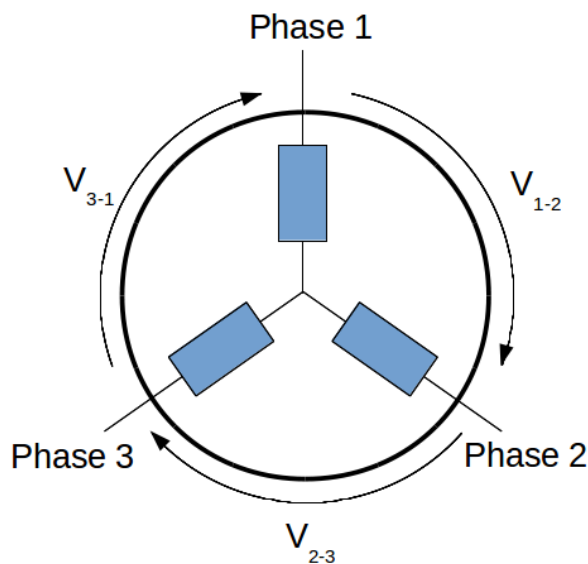The following notation will be used for the windings voltage:



## Clockwise commutation table


Phase	Hall sensors			Switches						Phases			Windings		
	H3	H2	H1	Q1L	Q1H	Q2L	Q2H	Q3L	Q3H	P1	P2	P3	$V_{1-2}$	$V_{2-3}$	$V_{3-1}$
I	1	0	1	0	1	1	0	0	0	$+V_m$	Gnd	NC	$-V_m$	-	-
II	0	0	1	0	1	0	0	1	0	$+V_m$	NC	Gnd	-	-	$+V_m$
III	0	1	1	0	0	0	1	1	0	NC	$+V_m$	Gnd	-	$-V_m$	-
IV	0	1	0	1	0	0	1	0	0	Gnd	$+V_m$	NC	$+V_m$	-	-
V	1	1	0	1	0	0	0	0	1	Gnd	NC	$+V_m$	-	-	$-V_m$
VI	1	0	0	0	0	1	0	0	1	NC	Gnd	$+V_m$	-	$+V_m$	-

We use cookies to ensure that we give you the best experience on our website. If you continue to use this site we will assume that you are happy with it.

1=Q1H 2=Q1L

3=Q2H 4=Q2L


5=Q3H 6=Q3L

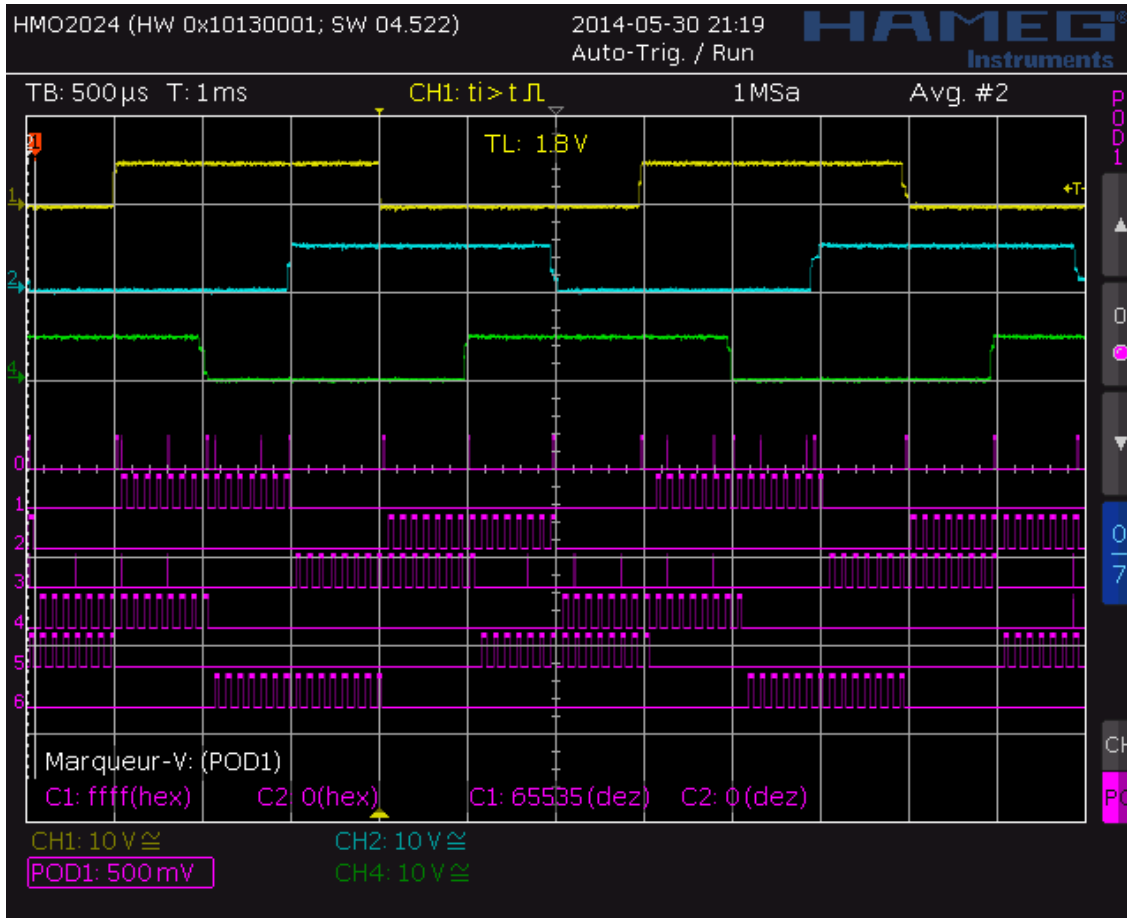

## Counter clockwise commutation table

Phase	Hall sensors			Switches						Phases			Windings		
	H3	H2	H1	Q1L	Q1H	Q2L	Q2H	Q3L	Q3H	P1	P2	P3	V <sub>1-2</sub>	V <sub>2-3</sub>	V <sub>3-1</sub>
VI	1	0	0	0	0	0	1	1	0	NC	+V <sub>m</sub>	Gnd	-	-V <sub>m</sub>	-
V	1	1	0	0	1	0	0	1	0	+V <sub>m</sub>	NC	Gnd	-	-	+V <sub>m</sub>
IV	0	1	0	0	1	1	0	0	0	+V <sub>m</sub>	Gnd	NC	-V <sub>m</sub>	-	-
III	0	1	1	0	0	1	0	0	1	NC	Gnd	+V <sub>m</sub>	-	+V <sub>m</sub>	-
II	0	0	1	1	0	0	0	0	1	Gnd	NC	+V <sub>m</sub>	-	-	-V <sub>m</sub>
I	1	0	1	1	0	0	1	0	0	Gnd	+V <sub>m</sub>	NC	+V <sub>m</sub>	-	-

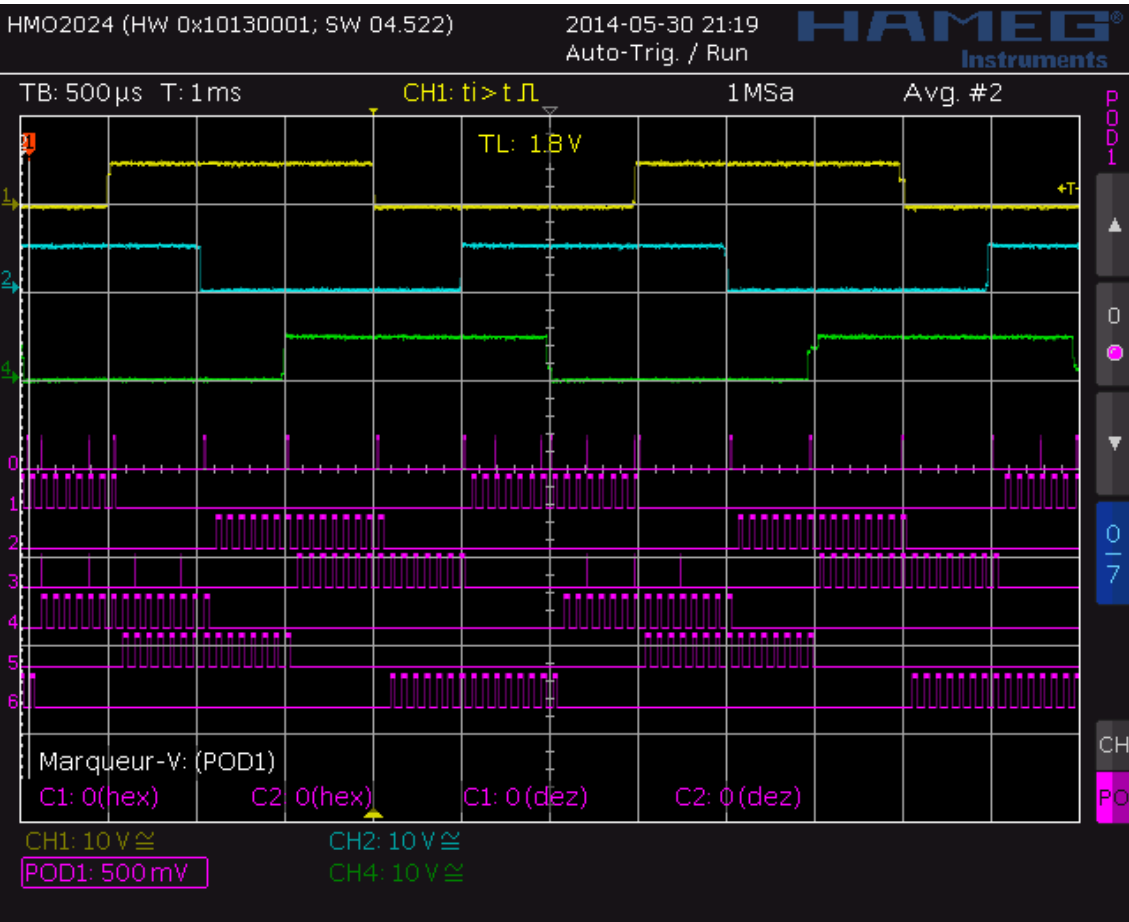Same capture as previously for counter clockwise:





**All components are from authorized distributors!**  
Reliable PCBA service for small&medium volume.



**Order Now**

5 thoughts on “Commutation sequence for BLDC motors using Hall effect position sensors”



June 2, 2016 at 3:23 pm

sir i want the code of this program. for microcontroller atmega32

ahsan



June 3, 2016 at 8:55 am

It has been developed for ATmega32M1. Have a look at this board :

We use cookies to ensure that we give you the best experience on our website. If you continue to use this site we will assume that you are happy with it.

Philippe  
Lucidarme



June 15, 2017 at 4:53 am

Can you tell me when should i use complementary PWMs for high and low legs.  
Currently you have used one pwm and the permanently LOW.

Learner



June 15, 2017 at 4:55 am

Also what is the frequency of PWM. On what factors should we select this  
frequency? Please suggest.

Learner



June 15, 2017 at 6:22 am

The frequency selection is dependent of several parameters. If the PWM is  
under 20KHz, it becomes audible, so  $F > 20\text{KHz}$ . Sometime, increasing the  
frequency ~100KHz create cross conduction in the transistors. Increase the  
frequency, but check the power consumption.

Philippe  
Lucidarme